 



Decoder



```
# vsim
# Start time: 20:45:58 on Sep 24, 2015
# Loading work.testDecoder
# Loading work.structuralDecoder
# En A0 A1 | O0 O1 O2 O3 | Expected Output
# 0 0 0 | 0 0 0 0 | All false
# 0 1 0 | 0 0 0 0 | All false
# 0 0 1 | 0 0 0 0 | All false
# 0 1 1 | 0 0 0 0 | All false
# 1 0 0 | 1 0 0 0 | O0 Only
# 1 1 0 | 0 1 0 0 | O1 Only
# 1 0 1 | 0 0 1 0 | O2 Only
# 1 1 1 | 0 0 0 1 | O3 Only
# 0 ns
# 8400 ns
```

This tests all possible cases for the Decoder. The results match the expected outcome.


Multiplexer

 

```
# vsim
# Start time: 21:14:55 on Sep 24, 2015
# Loading work.testMultiplexer
# Loading work.structuralMultiplexer
# A1 A0 | I3 I2 I1 I0 | O | Expected Output
# 0 0 | x x x 0 | 0 | 0
# 0 0 | x x x 1 | 1 | 1
# 0 1 | x x 0 x | 0 | 0
# 0 1 | x x 1 x | 1 | 1
# 1 0 | x 0 x x | 0 | 0
# 1 0 | x 1 x x | 1 | 1
# 1 1 | 0 x x x | 0 | 0
# 1 1 | 1 x x x | 1 | 1
# 0 ns
# 8400 ns
```

We only need to test the cases above, rather than every case because the multiplexer only chooses one input to pass through to the output. Therefore, the other inputs are non-essential.

Full Adder

 

```
# vsim
# Start time: 20:46:04 on Sep 24, 2015
# Loading work.testFullAdder
# Loading work.structuralFullAdder
# A B Ci | Co O | Expected Output
# 0 0 0 | 0 0 | 0 0
# 0 0 1 | 0 1 | 0 1
# 1 0 0 | 0 1 | 0 1
# 1 0 1 | 1 0 | 1 0
# 0 1 0 | 0 1 | 0 1
# 0 1 1 | 1 0 | 1 0
# 1 1 0 | 1 0 | 1 0
# 1 1 1 | 1 1 | 1 1
# 0 ns
# 8400 ns
```

This tests every possible case for the Full Adder. There is a slight timing anomaly that can be seen in the wave form graph above.